

Losses in Loudspeakers



Claus Futtrup, MSc M.E.
Chief Technical Officer


Traditionally loudspeaker designs are simulated with electrical equivalent circuit following the Thiele/S

To see how good or bad the model is, let's build a box and measure, then compare to simulations.

Test box - essentially lossless:



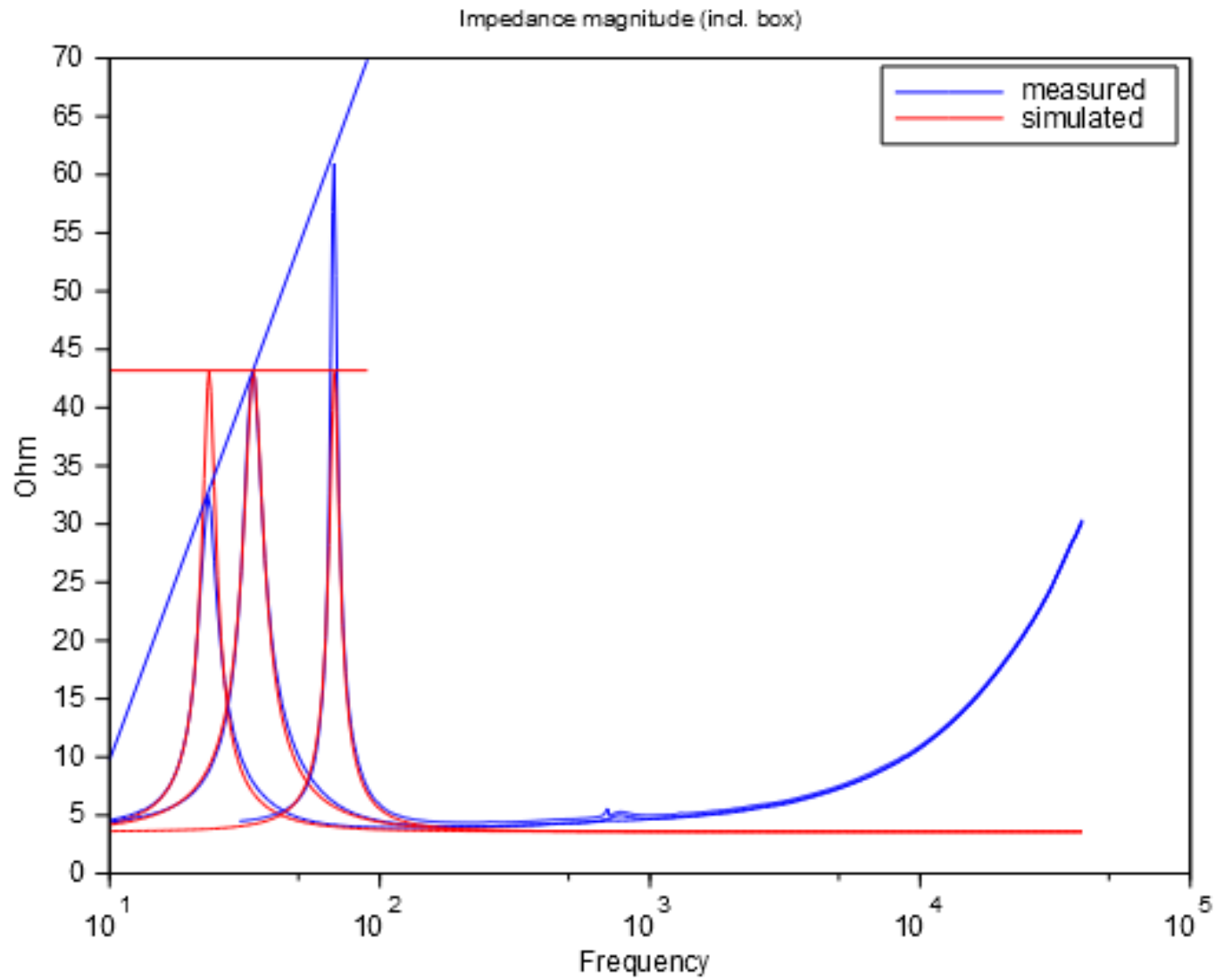
3 measurements, compared to 3 simulations (Thiele/



Simulations do not match real-world at all!

Why not?

What shall
we
do about
it?

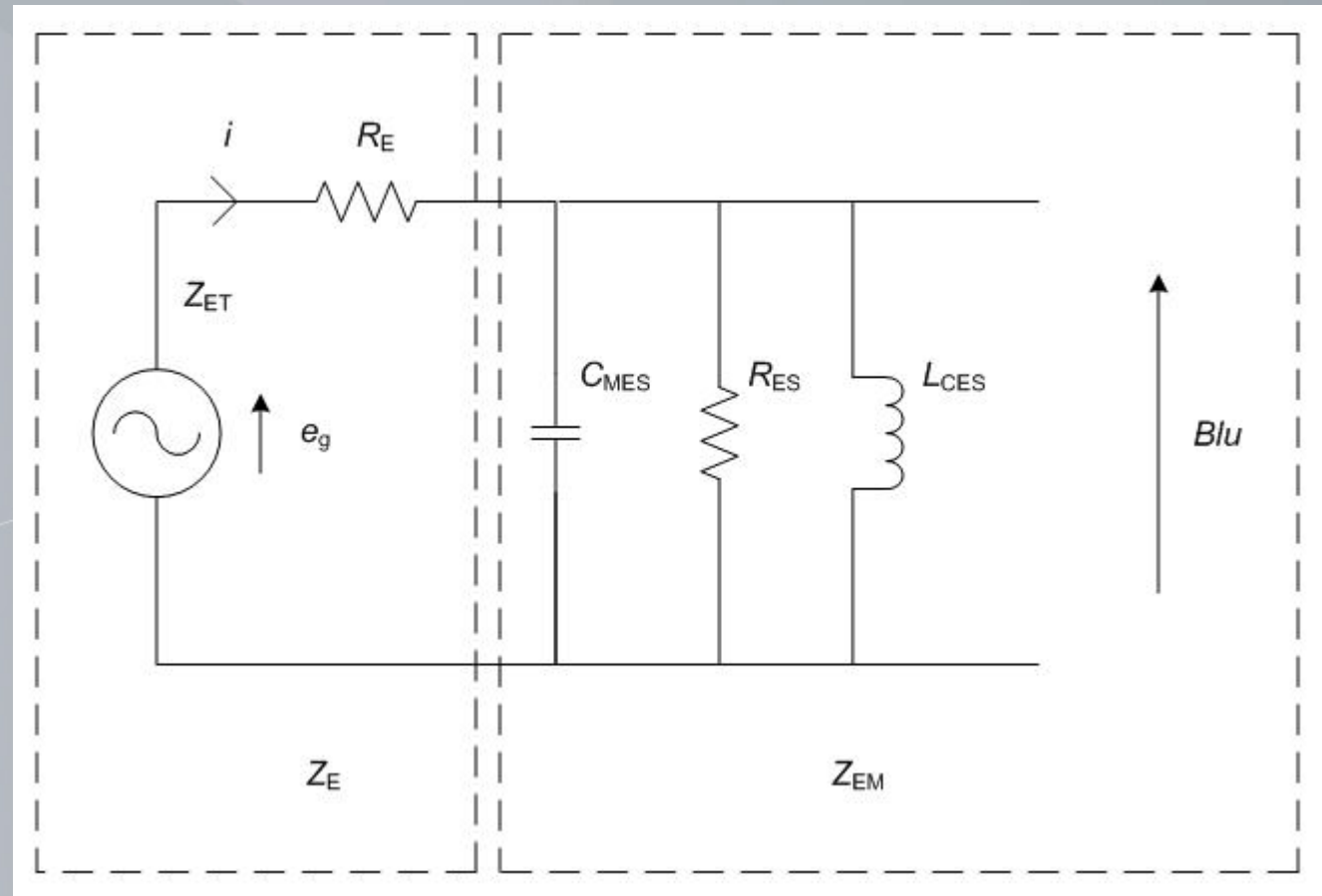

Richard Small on Q_l , Q_p and Q_a - conclusions

Q_p – between 50 and 100

Q_a – typically 100 or more

Q_l – between 5 and 20


Link to paper ([PDF](#)) page 5

Small is looking for an explanation in the system enclosure – but the actual cause shall be found in the transducer.

Quote: The last result is surprising, because the enclosure tested well built and appeared to be leak free...

Quote: ... leads to the conclusion that the measured leakage in apparently leak-free systems is not an error of measurement but an indication that the actual losses in the system enclosure is not constant with frequency...

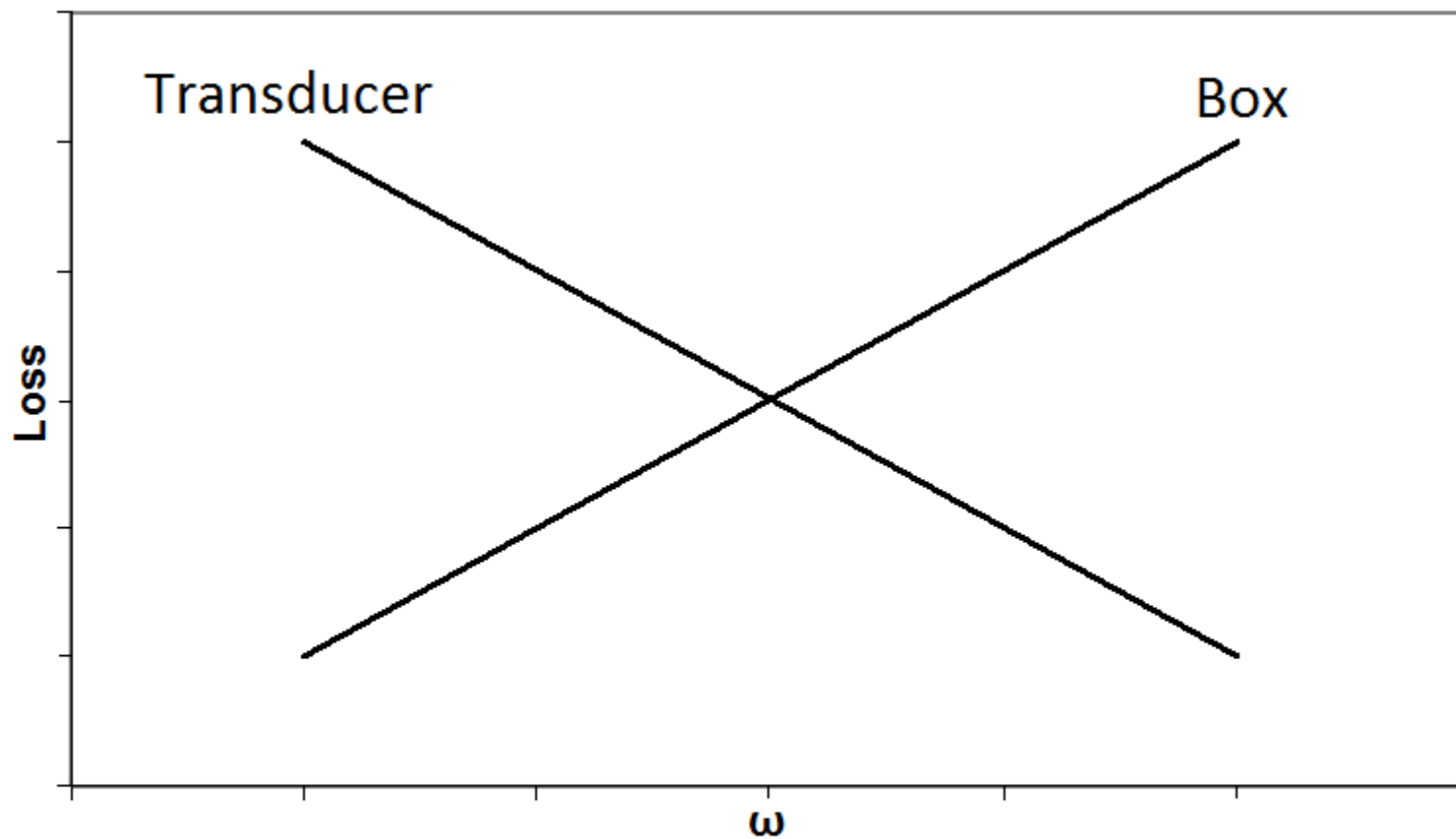Losses, $Q_1 = 7$: A mix of Q_a and transducer admittance



Good vs. bad models

		Transducer model	
		Without freq. dep. damping	With frequency dep. damping
Box model	Without stuffing	✓	✗
	With stuffing	✗	✓

The conclusion is valid for all models, also State Variable Models, Finite Element Models, et


The end.

Questions?

For more info see: <http://www.cfuttrup.com>


(I have some "bonus" slides, if we have time)

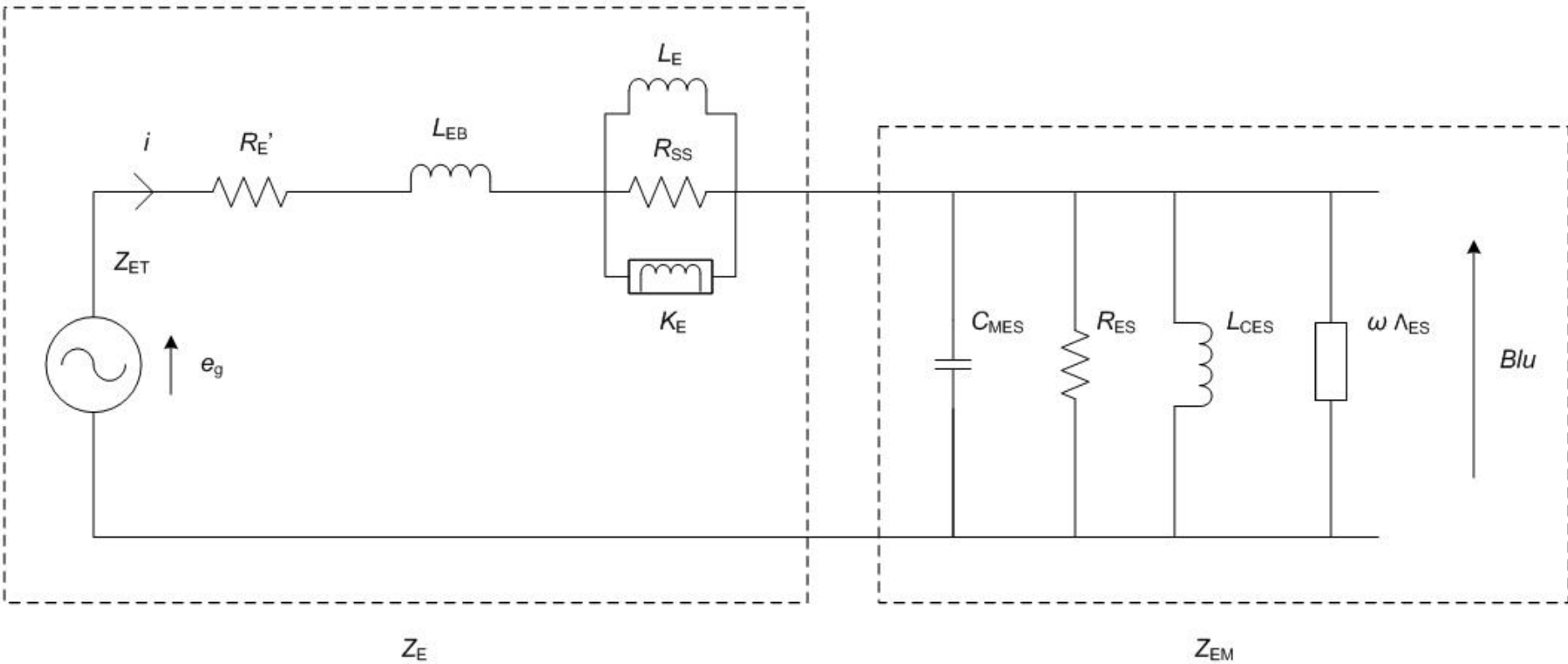Transducer model including frequency dependent dampi



Model proposed by Thorborg and Futtrup

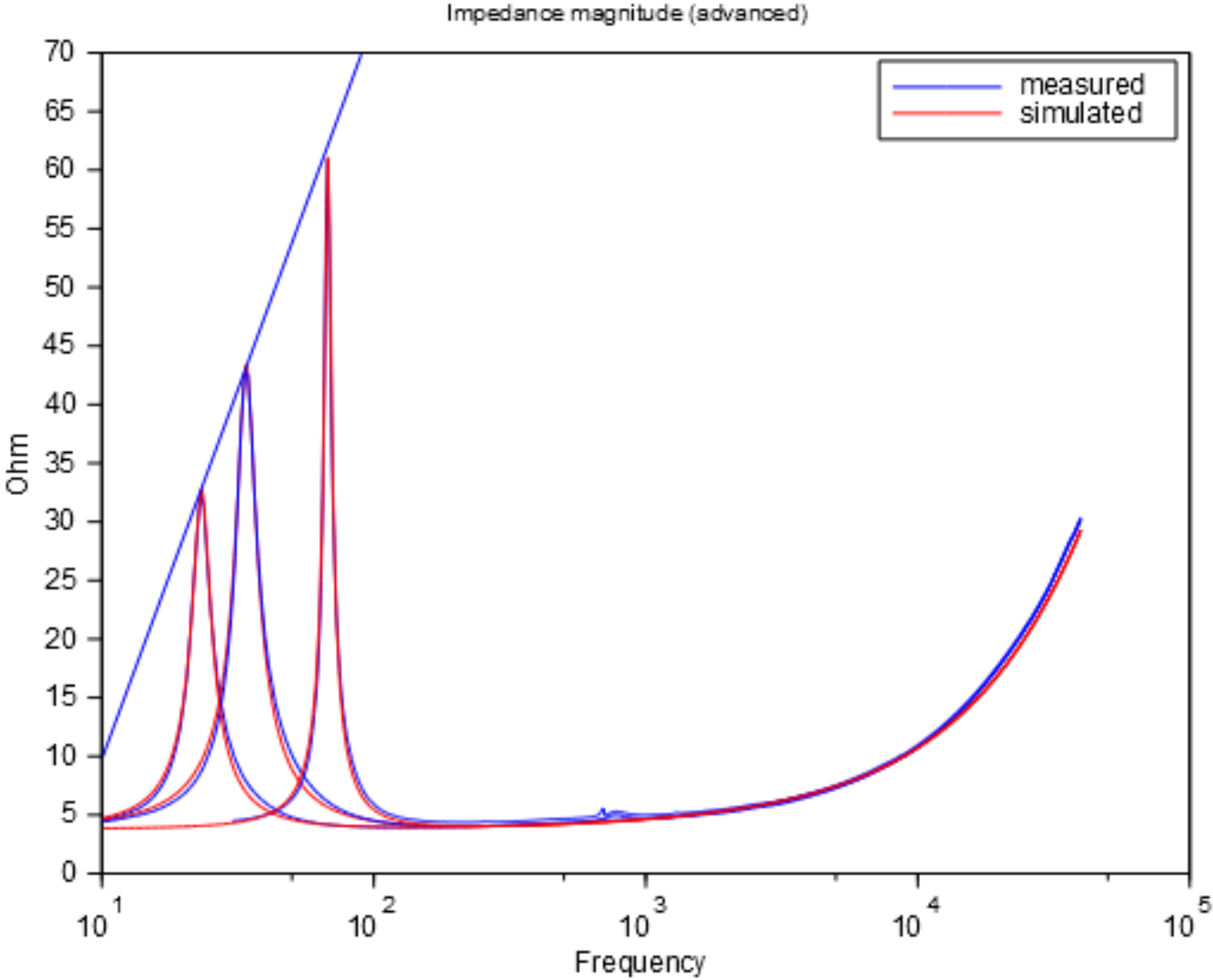Measurements and simulations - using the proposed mo



What does the box model look like?


When the transducer includes frequency dependent damping then the box model must include effects of damping m

Source:


<http://www.aes.org/e-lib/browse.cfm?elib=15791>

Link: ([PDF](#))

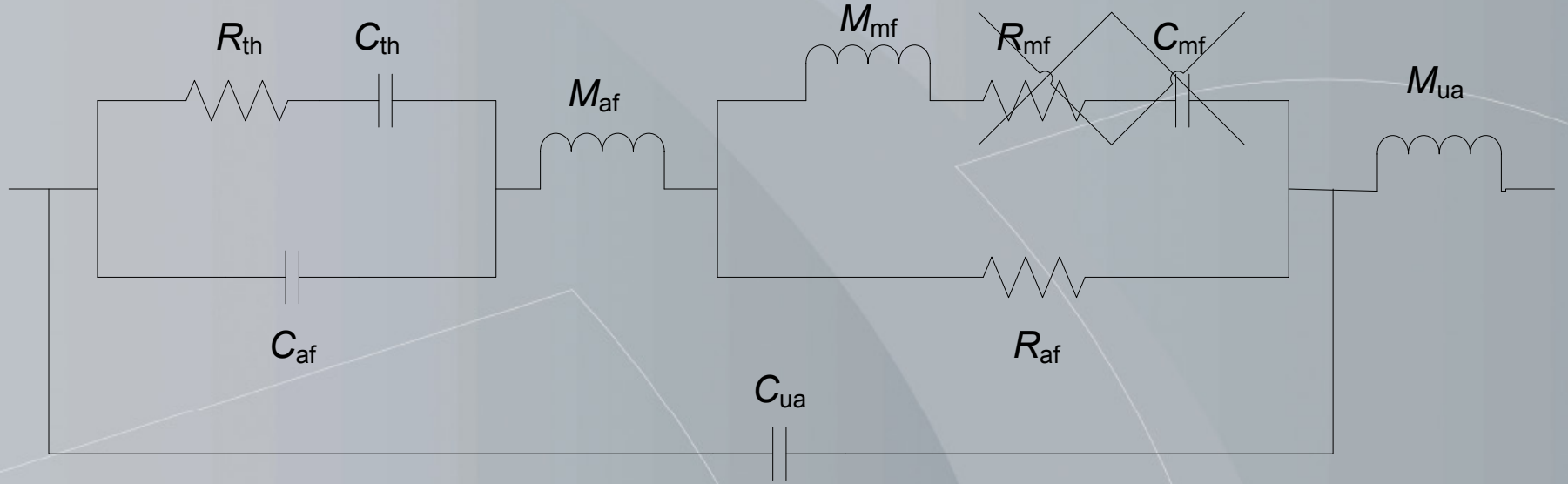
Model of damping material (mechanical domain)



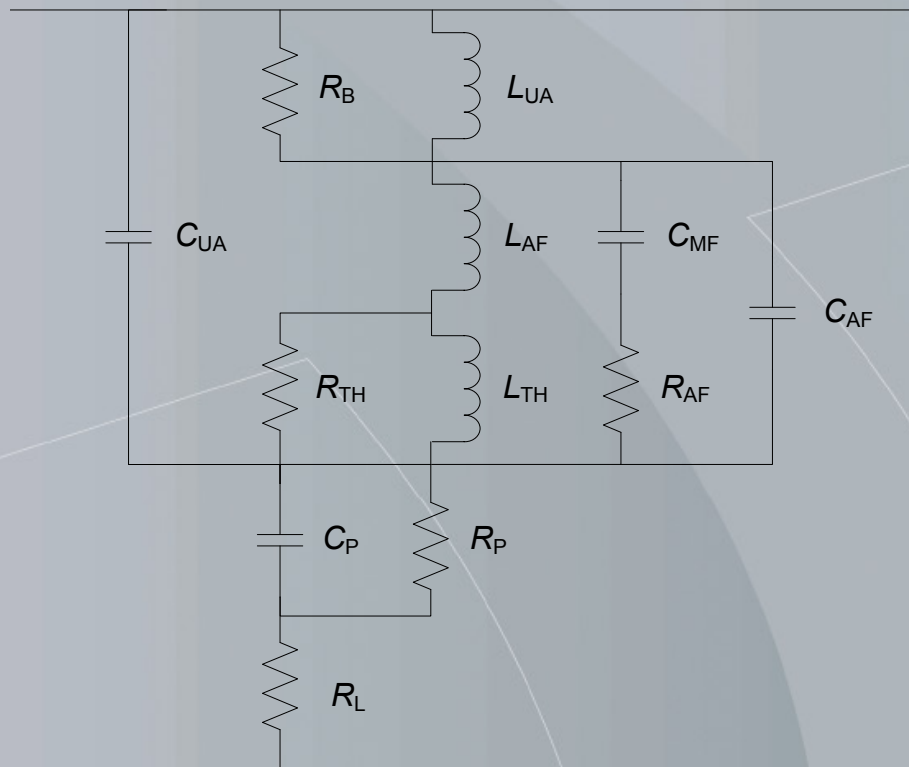Box mode, Electrical Equivalent, with R_b



Volume expansion graph

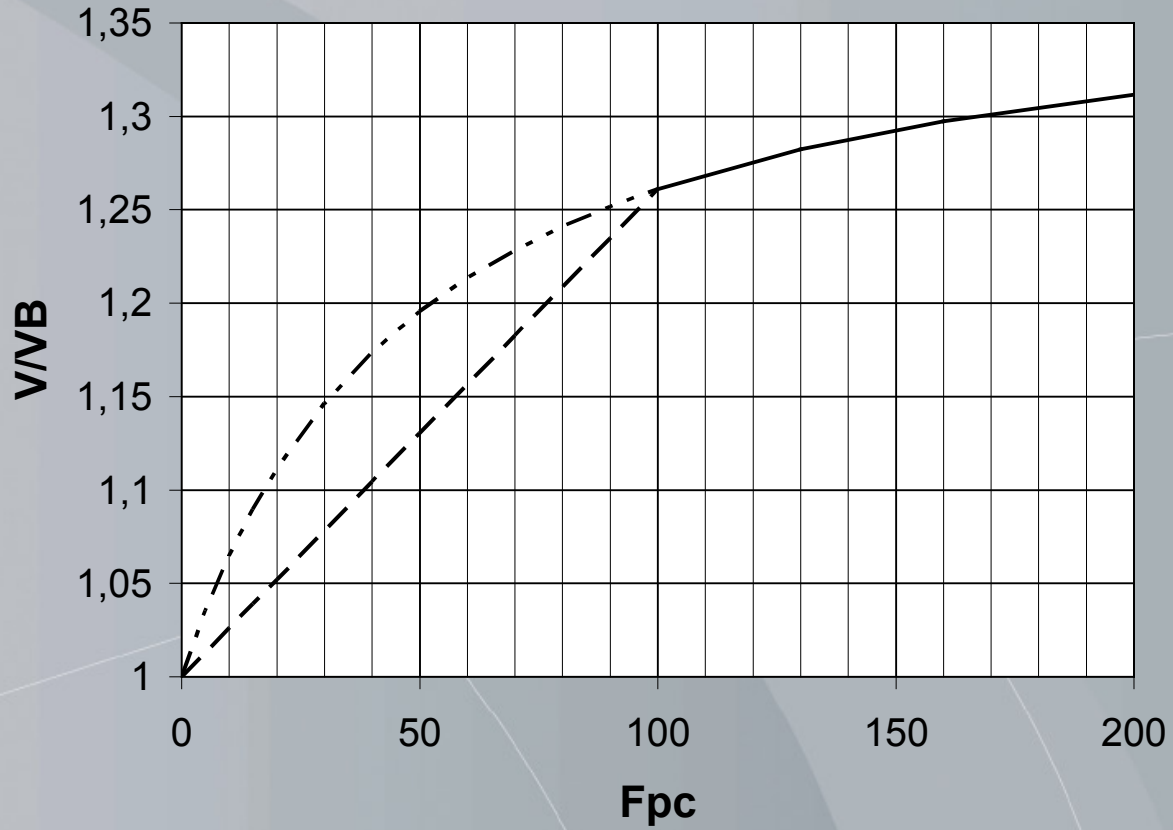

Mechanical model, Tarnow

$$\begin{aligned} R_f = \lambda &= R_{cr}^{2/3} \cdot R_{lr}^{1/3} \\ &= \frac{16 \cdot \eta}{d_f^2} \cdot \frac{f}{0,806 \cdot LN(1/f) - 0,929 + 1,26 \cdot f} \end{aligned}$$

Thank you.

Questions?

Claus Futtrup

futtrup@seas.no